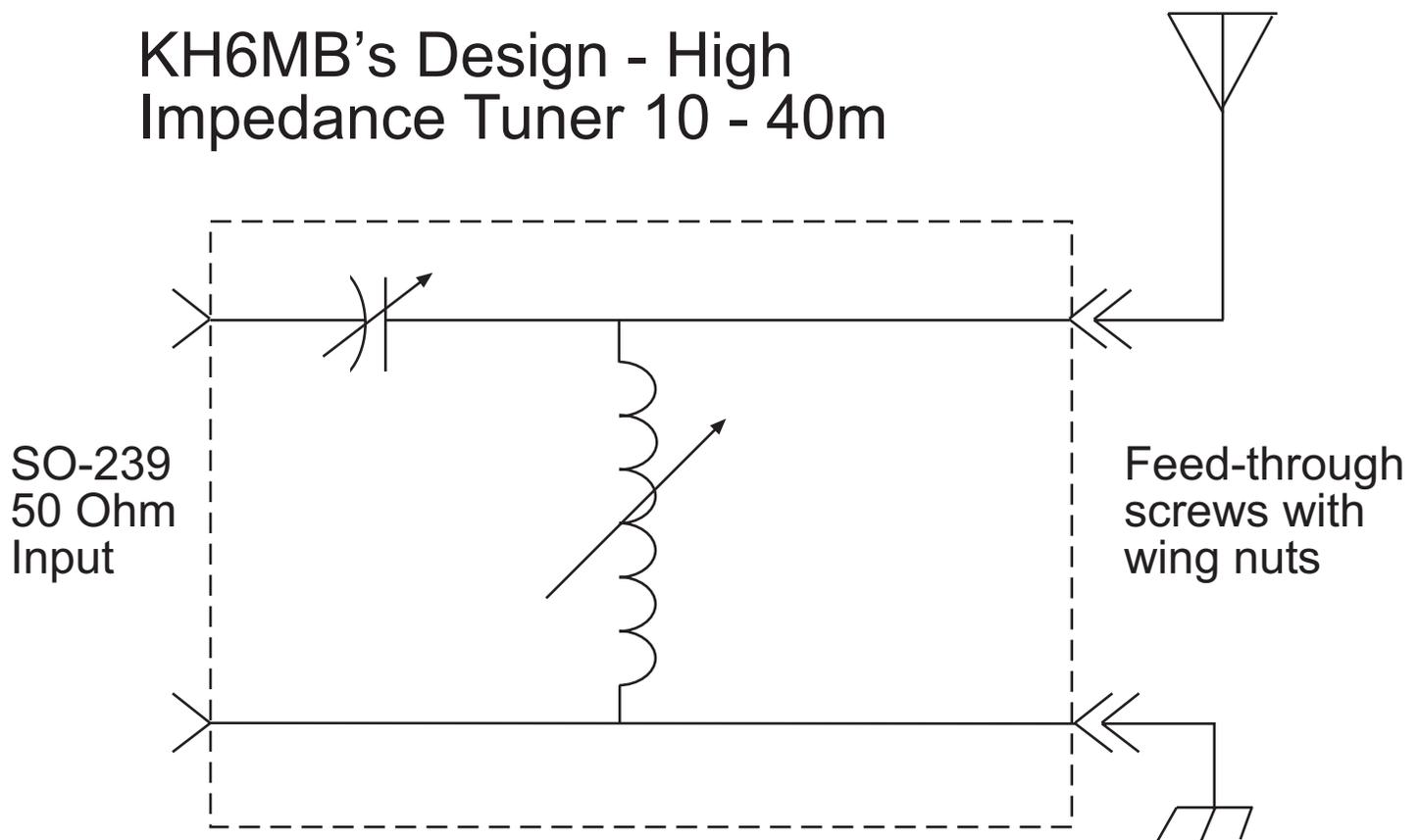


KH6MB's Design - High Impedance Tuner 10 - 40m



Variable Capacitor: 5.5 -85 pF 4500 Vpk
Variable Inductor: 0.1 - 20 uH 4500 Vpk

End feed vertical dipoles, half-squares or
(center lead of bobtail curtains).

A 4 to 5 square foot piece of hardware cloth
(ex.1/4" square mesh) serves as ground.